

## Pre-Lab Questions

### Part 1


1. This design required an instruction register because we have two separate states. We have a fetch state that loads the opcode and then a separate state that executes that particular opcode. Because both of these states happen in separate clock cycle we need a register to remember these values. Additionally, the IR allows us to have opcodes that have their own states. Such as with LDAA #data and JMP Addr in part2.
2. You could add a program counter that stores the current location in memory and then increments with each clock cycle. So each cycle the correct address from memory would be loaded.
3. To have more instructions we could simply use a bigger Instruction Register. More bits allows us to have more instructions. A 3 bit register would allow for 8 instructions.

### Part 2

1. LDAA and JMP require separate states in part 2 because the our design allows us to only load 4 bits at a time from memory. If we had a bigger memory bus and PC we could load the data for LDAA and JMP in the same clock cycle.
2. In order to change the address lines to start at \$5370 instead of \$3AB0 we would need to change the configuration of the the first 11 bits. Currently the address bus has the first 11 bits set to 01110101011 through the use of Ground and VCC. However in order to change this to point to location \$5370 we need to change the first 11 bits to be 010100110111.

## Part 1 Pre-Lab Materials


### Part 1 asm

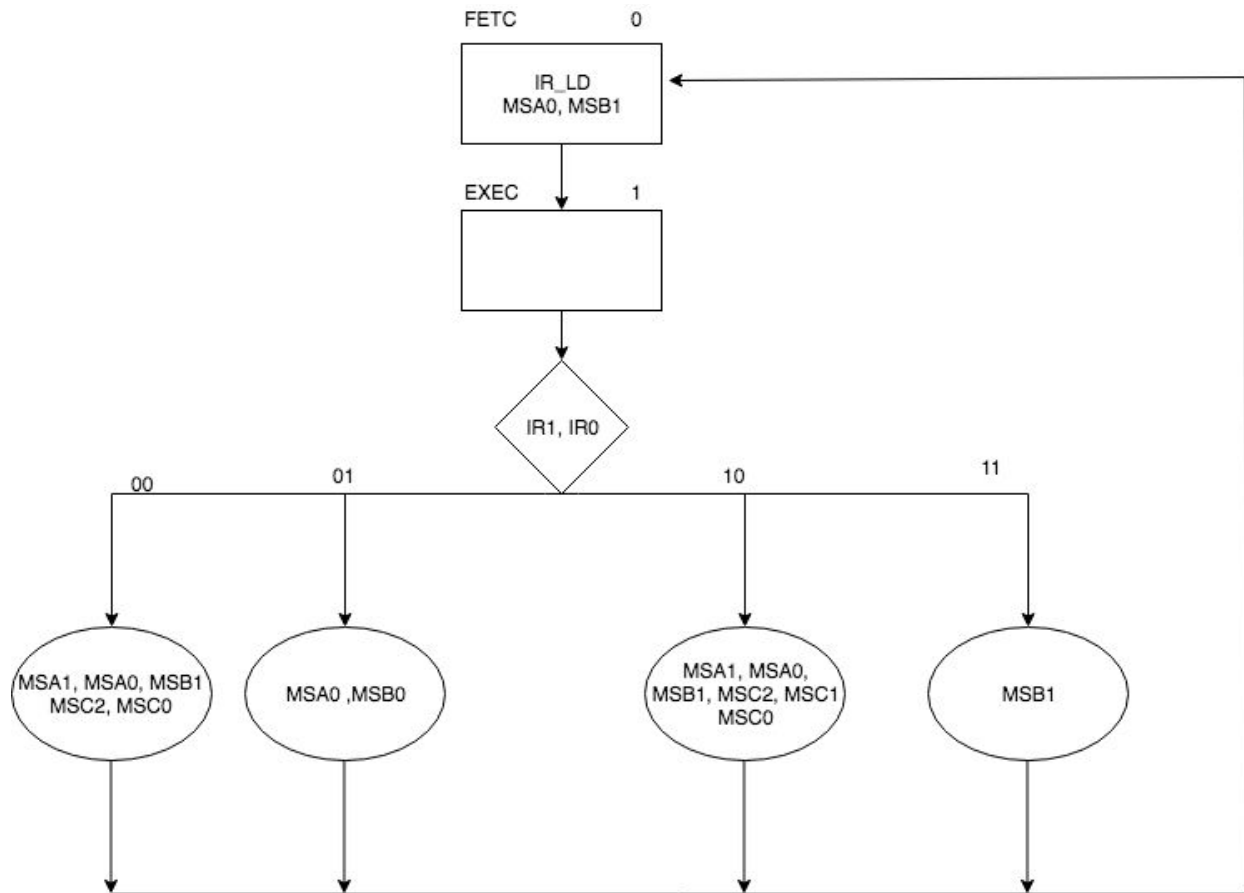


### Part 1 Next State Truth Table

STATE	Q	IR1:0	IR.LD	MSA1:0	MSB1:0	MSC2:0	STATE+	Q+
FETCH	0	XX	1	01	10	000	EXEC	1
EXEC	1	00	0	11	10	101	FETCH	0
EXEC	1	01	0	01	01	000	FETCH	0
EXEC	1	10	0	11	10	111	FETCH	0
EXEC	1	11	0	00	10	000	FETCH	0

## Part 1 Design

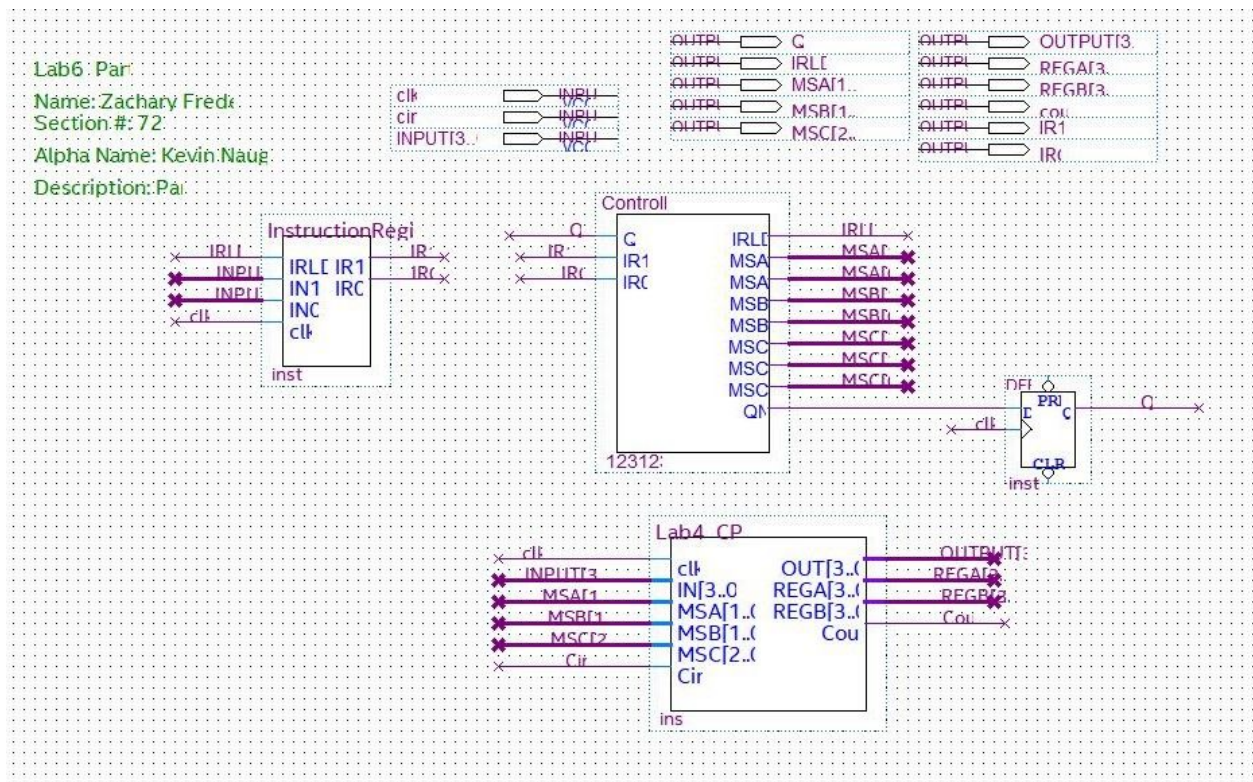

## Part 1 Simulation

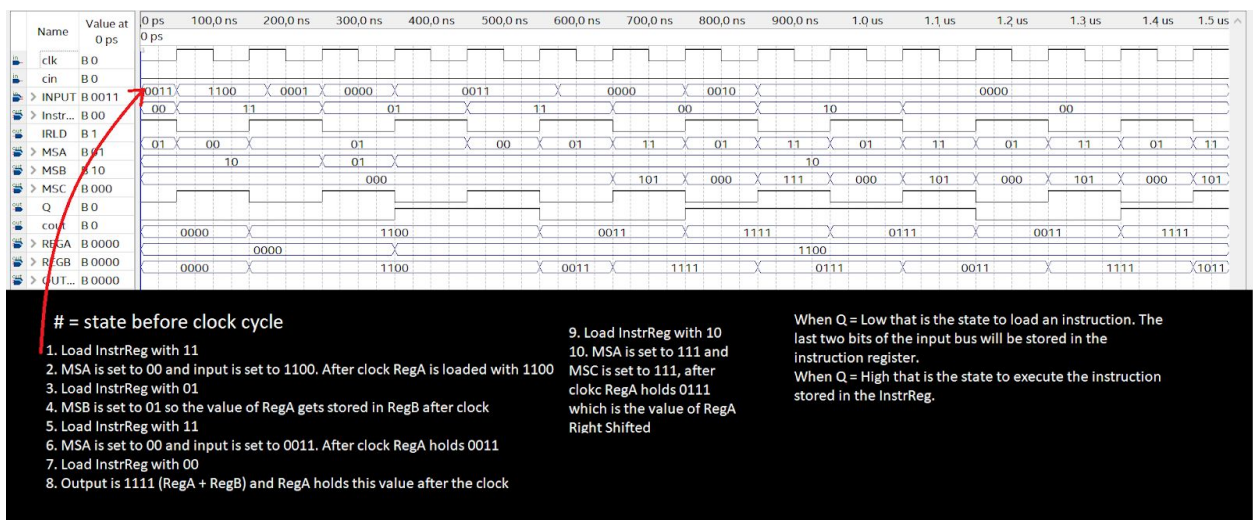

## Part 1 Code

```
--Lab: 6 Part 1
--Name: Zachary Frederick
--Section: 7287
--TA: KN
--Description: Controller vhd1 code


entity Controller is port(
    Q, IR1, IR0: IN BIT;
    IRLD, MSA1, MSA0, MSB1, MSB0: OUT BIT;
    MSC2, MSC1, MSC0: OUT BIT;
    QN: OUT BIT);
end Controller;

Architecture Behavior of Controller is
begin

    QN    <= NOT Q;
    IRLD  <= NOT Q;
    MSA1  <= (Q AND NOT IR1 AND NOT IR0) OR (Q AND IR1 AND NOT IR0);
    MSA0  <= NOT Q OR NOT IR1 OR NOT IR0;
    MSB1  <= NOT Q OR IR1 OR NOT IR0;
    MSB0  <= Q AND NOT IR1 AND IR0;
    MSC2  <= (Q AND NOT IR1 AND NOT IR0) OR (Q AND IR1 AND NOT IR0);
    MSC1  <= Q AND IR1 AND NOT IR0;
    MSC0  <= (Q AND NOT IR1 AND NOT IR0) OR (Q AND IR1 AND NOT IR0);

end Behavior;
```
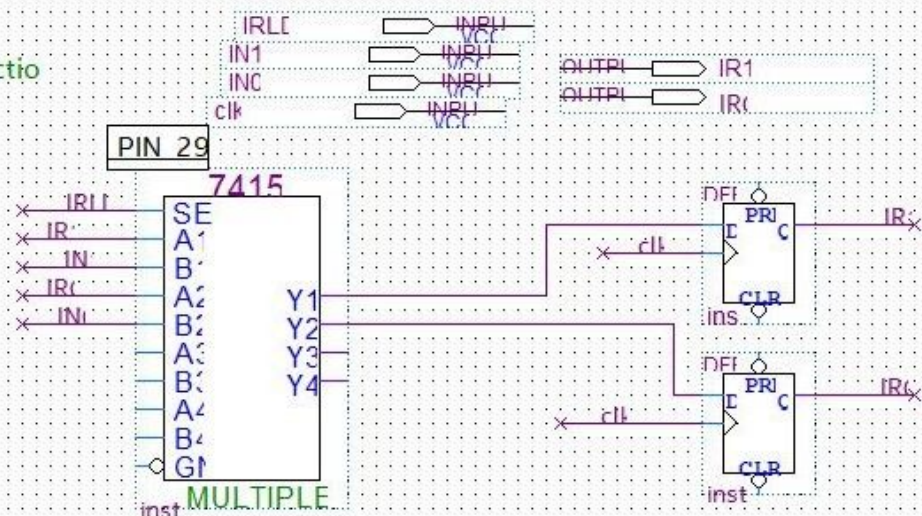
```
--Lab: 6: Part
--Name: Zachary Frede
--Section: 72:
--TA: K:
--Description: Instructio
```





















# Lab4: CP

Name: Zachary Fredr


Section #: 72

Alpha Name: Kevin Naug

Description: CPU with F

                


## Part 2

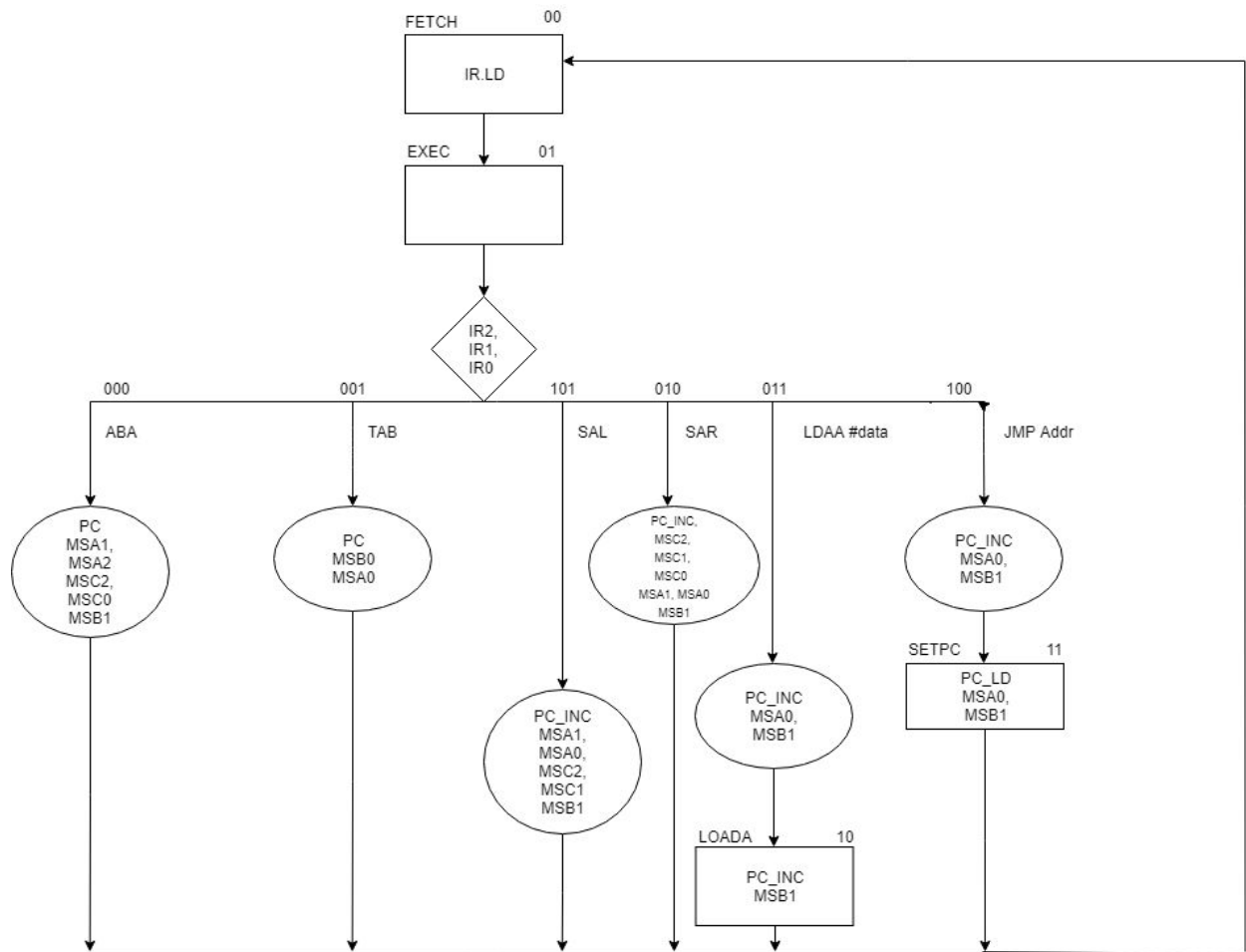




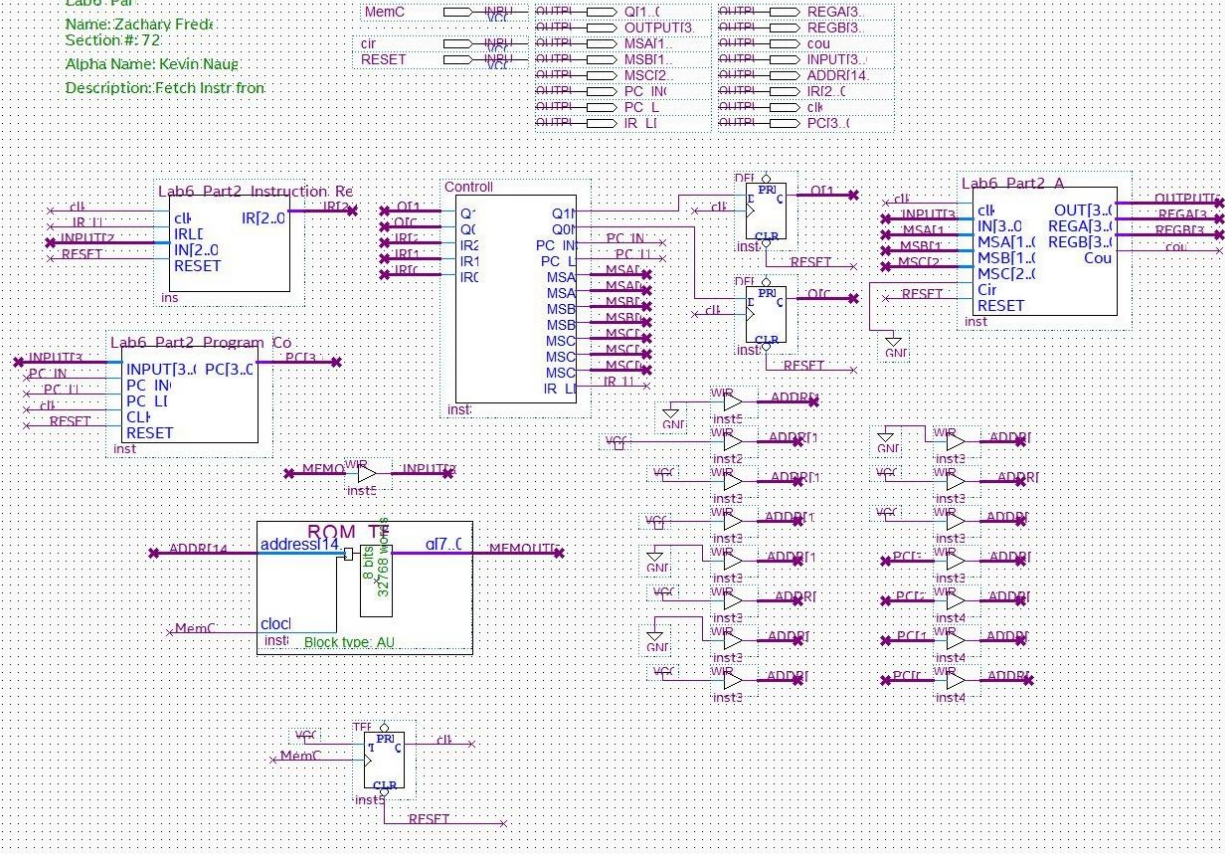Lab6\_Par  
 Name: Zachary Fredi  
 Section #: 72  
 Alpha Name: Kevin Naug  
 Description: Fetch Instr from



## Simulation

 

Pay attention to Input, RegA, RegB and the instruction register. Prior to first clock set Reset\_L low to reset CPU.

- During the first fetch state we load 0011 from input to 011 in the IR. On the next cycle we set input to 1111 and load that value into RegA.
- After this we set the input to 010 which is the SAR opcode. This causes the value of RegA to be shifted from 1111 to 0111.
- Input is set to 001 which causes the value of RegA to be transferred to RegB.
- After this we input 011 and also set input to 100. This loads 4 into RegA.
- The next instruction 000 which sums RegA and RegB and stores it in RegA. This sets RegA to 1011 or 11.

- The next instruction is 101 which is SAL. This shifts the value in RegA left. RegA updates from 1011 to 0110.
- The next instruction is 010 which is jump to address \$3AB2 which sets the PC to 0010. After this the same sequence repeats. The code continues to execute instructions from \$3AB0 to \$3AB9 endlessly.

If comparing the values of Input, IR, RegA, and RegB to the hand assembled table you can see that the computer is operating correctly

Next State Truth Table

STATE	Q1	Q0	IR2	IR1	IR0	IR_LD	PC_INC	PC_L D	MSA 1	MSA 0	MSB 1	MSB 0	MSC 2	MSC 1	MSC 0	STATE+	Q1+	Q0+
FETCH	0	0	X	X	X	1	0	0	0	1	1	0	0	0	0	EXEC	0	1
EXEC	0	1	0	0	0	0	1	0	1	1	1	0	1	0	1	FETCH	0	0
EXEC	0	1	0	0	1	0	1	0	0	1	0	1	0	0	0	FETCH	0	0
EXEC	0	1	0	1	0	0	1	0	1	1	1	0	1	1	1	FETCH	0	0
EXEC	0	1	0	1	1	0	1	0	0	1	1	0	0	0	0	LOADA	1	0
EXEC	0	1	1	0	0	0	1	0	0	1	1	0	0	0	0	SETPC	1	1
EXEC	0	1	1	0	1	0	1	0	1	1	1	0	1	1	0	FETCH	0	0
LOADA	1	0	X	X	X	0	1	0	0	0	1	0	0	0	0	FETCH	0	0
SETPC	1	1	X	X	X	0	0	1	0	1	1	0	0	0	0	FETCH	0	0


Instruction Register

Lab6 Part

Name: Zachary Fred  
Section #: 72

Alpha Name: Kevin Naug

Description: Instruction

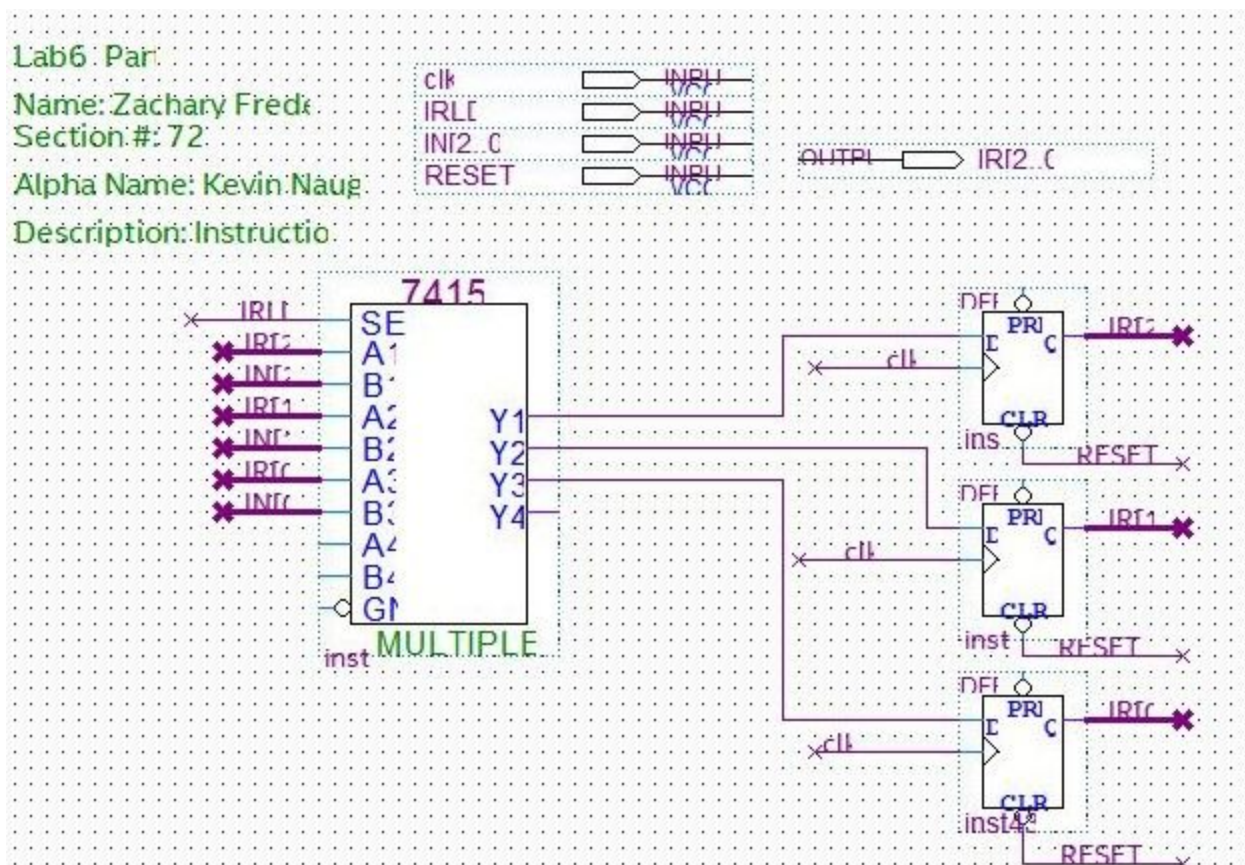



## Program Counter


Lab6 Part

Name: Zachary Frederick

Section #: 72

Alpha Name: Kevin Naug

Description: Program Co

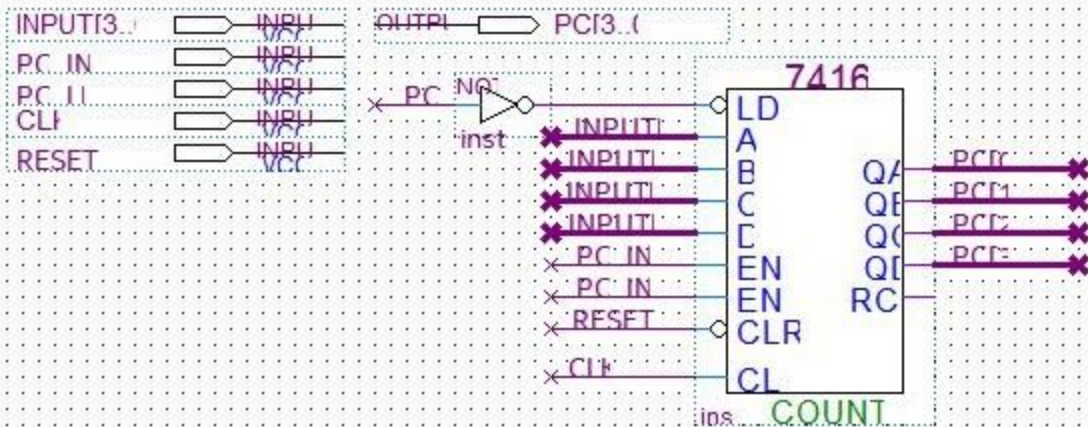


## Controller Code

```
--Lab6_Part2
--Name: Zachary Frederick
--Section #: 7287
--Alpha Name: Kevin Naughton
--Description: Controller for CPU
entity Controller is port(
    Q1, Q0: IN BIT;
    IR2, IR1, IR0: IN BIT;
    Q1N, Q0N: OUT BIT;
    PC_INC, PC_LD: OUT BIT;
    MSA1, MSA0: OUT BIT;
    MSB1, MSB0: OUT BIT;
    MSC2, MSC1, MSC0: OUT BIT;
    IR_LD: OUT BIT);
end Controller;
Architecture Behavior of Controller is
begin
    Q1N <= (NOT Q1 AND Q0 AND NOT IR2 AND IR1 AND IR0) OR (NOT Q1 AND Q0 AND IR2 AND NOT IR1 AND NOT IR0);
    Q0N <= (NOT Q1 AND NOT Q0) OR (NOT Q1 AND Q0 AND IR2 AND NOT IR1 AND NOT IR0);
    IR_LD <= (NOT Q1 AND NOT Q0);
    PC_INC <= (Q1 OR Q0) AND (NOT Q1 OR NOT Q0);
    PC_LD <= Q1 AND Q0;
    MSA1 <= (NOT Q1 AND Q0 AND NOT IR2 AND NOT IR1 AND NOT IR0)
    OR (NOT Q1 AND Q0 AND NOT IR2 AND IR1 AND NOT IR0)
    OR (NOT Q1 AND Q0 AND IR2 AND NOT IR1 AND NOT IR0);
    MSA0 <= NOT Q1 OR Q0;
    MSB1 <= Q1 OR NOT Q0 OR IR2 OR IR1 OR NOT IR0;
    MSB0 <= NOT Q1 AND Q0 AND NOT IR2 AND NOT IR1 AND IR0;
    MSC2 <= (NOT Q1 AND Q0 AND NOT IR2 AND NOT IR1 AND NOT IR0)
    OR (NOT Q1 AND Q0 AND NOT IR2 AND IR1 AND NOT IR0)
    OR (NOT Q1 AND Q0 AND IR2 AND NOT IR1 AND NOT IR0);
    MSC1 <= (NOT Q1 AND Q0 AND NOT IR2 AND IR1 AND NOT IR0)
    OR (NOT Q1 AND Q0 AND IR2 AND NOT IR1 AND NOT IR0);
    MSC0 <= (NOT Q1 AND Q0 AND NOT IR2 AND NOT IR1 AND NOT IR0)
    OR (NOT Q1 AND Q0 AND NOT IR2 AND IR1 AND NOT IR0);
end Behavior;
```

# Assembly table

Address	Instruction	Machine Code	A	B	A	B	A	B	A	B
\$3AB0	LDAA \$15	\$3 \$F	\$1 5	-	-	-	-	-	-	-
\$3AB2	SAR	\$2	\$7	-	\$3	\$7	\$7	\$3	\$3	\$7
\$3AB3	TAB	\$1	\$7	\$7	\$3	\$3	\$7	\$7	\$3	\$3
\$3AB4	LDAA #4	\$3 \$4	\$4	\$7	\$4	\$3	\$4	\$7	\$4	\$3
\$3AB6	ABA	\$0	\$B	\$7	\$7	\$3	\$B	\$7	\$7	\$3
\$3AB7	SAL	\$5	\$6	\$7	\$E	\$3	\$6	\$7	\$E	\$3
\$3AB8	JMP 2	\$4 \$2	\$6	\$7	\$E	\$3	\$6	\$7	\$E	\$3
\$3ABA	TAB	\$1	-	-	-	-	-	-	-	-

## Lab6\_Part2\_Ext\_Rom Design

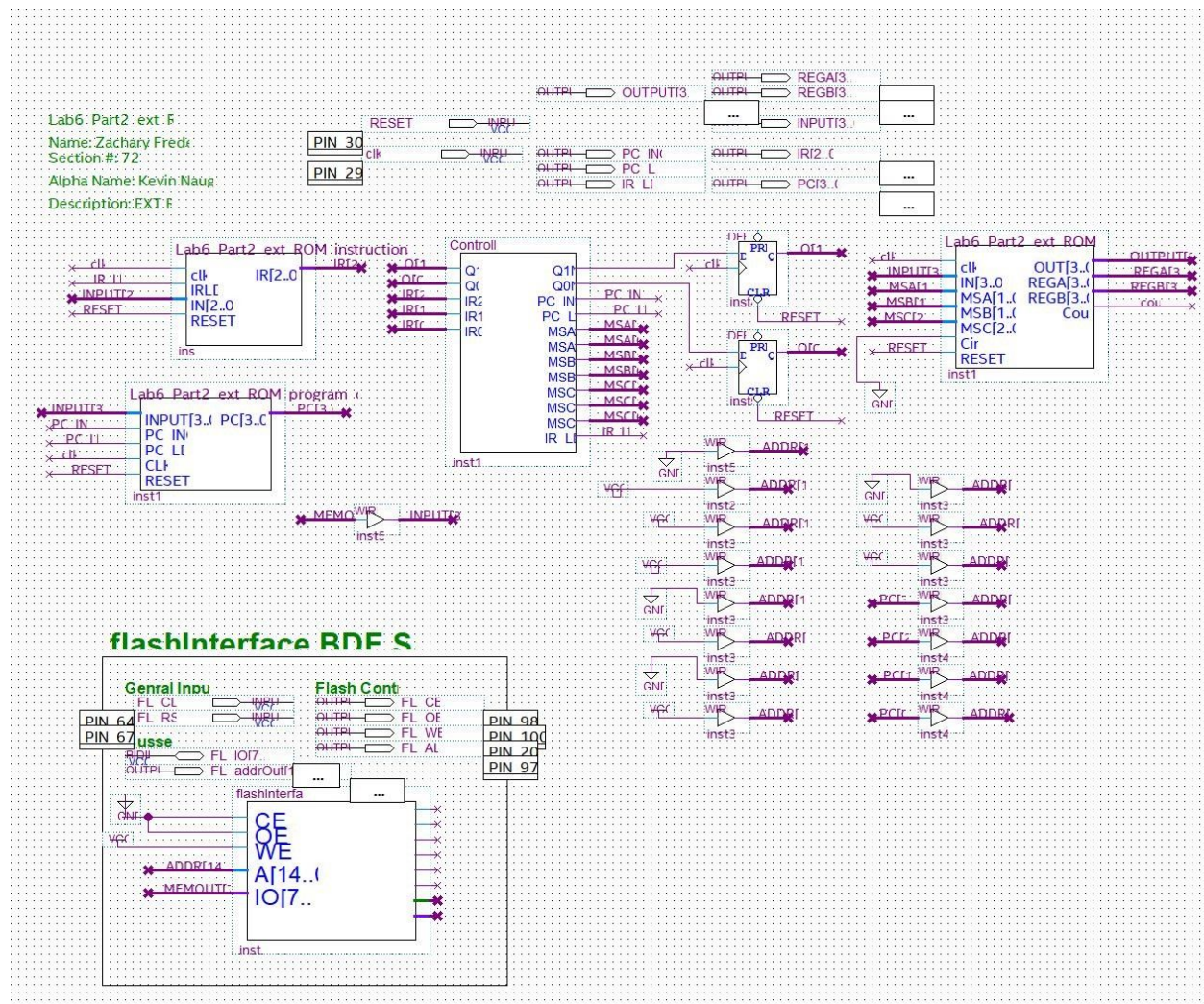

### Problems Encountered

No major problems were encountered. Everything went smoothly with this lab.

### Future Work

I would be interested in expanding the instruction register for more opcodes and a bigger memory bus to be able to load more data at once.